

## HOMEBREW A BALUN

Many modern HF transceivers come fully equipped with built in tuners. While these tuners are great for changing bands, the manufacturers left out a very important accessory; the 4 to 1 balun. Without a balun the transceiver can only feed an antenna which uses coaxial cable. While this may be satisfactory for some operators, this is a real problem for those of us who prefer the super low loss ladder line. The only other alternative is to buy an external tuner with a built-in balun which is really absurd after spending the additional money to have one built into the radio. Fortunately, a 4 to 1 balun can be easily home brewed as illustrated in Figures 1 and 2.

Figure 1 shows a bifilar winding on a toroid. The toroid should be type 2 (red) material and can be any of the following sizes but the number of bifilar turns should be adjusted accordingly:

TOROID	NUMBER OF TURNS	POWER RATING
T80-2	25	60 Watts
T106-2	16	100 Watts
T130-2	18	150 Watts
T157-2	16	250 Watts
T200-2	17	400 Watts
T200A-2	13	400 Watts
T400-2	14	1000 Watts

The exact number of turns is not critical but the numbers listed in the preceding table should yield optimum results. It is possible to exceed the power ratings listed above but the performance of the balun may be degraded during high SWR causing heating of the core.

Toroids of this type are available from Palomar Engineers, P.O. Box 462222, Escondido, CA 92046 (1-800-883-7020). If enough inquiries are made, the author will make a limited number of toroids available at RASON meetings for those who hate mail order. The author will even wind the toroid for the faint of heart.

The balun should be housed in a suitable metal enclosure such as those available at Radio Shack. Use a SO239 or BNC connector for the unbalanced input. Nylon binding posts such as RS 274-662 work just fine for the balanced output.

DE N1HFX

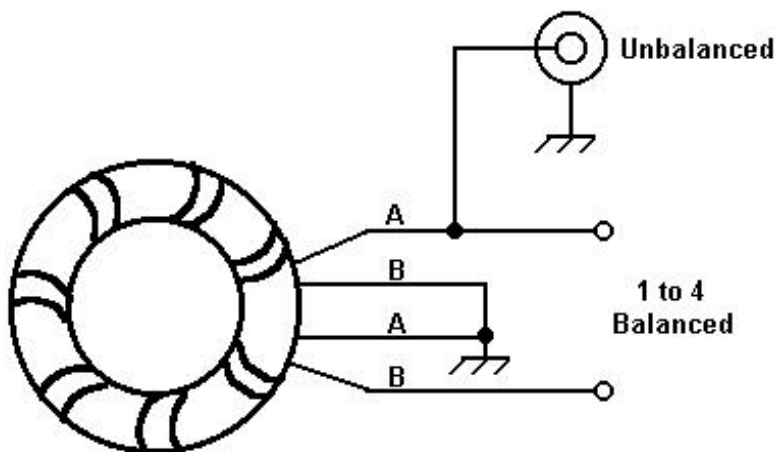


Figure 1

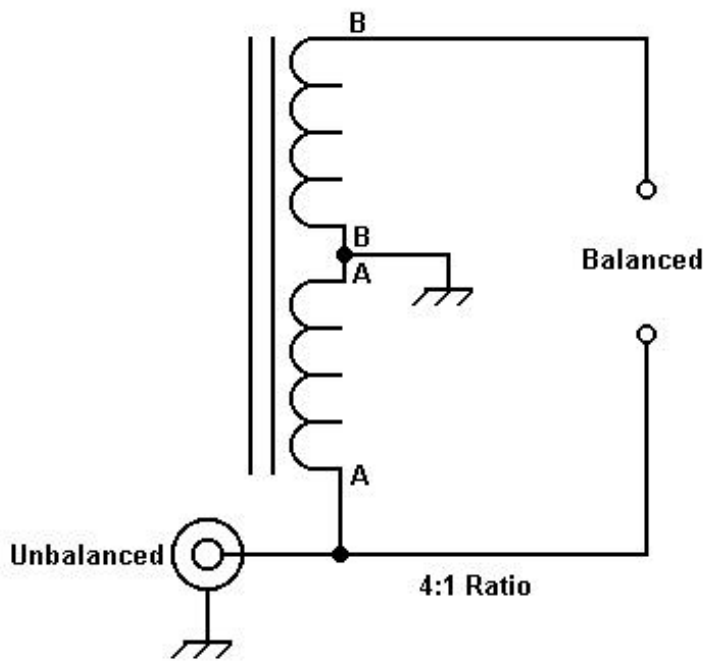


Figure 2